

# Extreme Value Analysis of an Electrical Circuit

## ▼ Introduction

An electrical component, such as a resistor or capacitor, is usually quantified with a nominal value and a tolerance. That is, a resistor could be rated at  $5\ \Omega$  with a tolerance of 5%; this means the resistance could vary between  $4.75$  and  $5.25\ \Omega$ .


Given the number of components in a circuit and their compounded tolerances, the actual performance of a circuit may not necessarily match its desired performance. This is a source of risk that needs to be managed and mitigated.

Accordingly, electrical engineers need to analyze a circuit over all potential operating conditions.

Extreme Value Analysis (EVA) is a process in which the behavior of a circuit is simulated for every permutation of extreme component parameters - that is, a resistor of  $5\ \Omega \pm 5\%$  is simulated at  $4.75\ \Omega$  and  $5.25\ \Omega$ , in combination with every permutation of extreme values for all other components (this is a type of [worst case circuit analysis](#)).

Given the results of an EVA, a circuit that falls out of spec may have its performance improved by replacing cheaper components that have a loose tolerance with higher quality components that have a tighter tolerance.

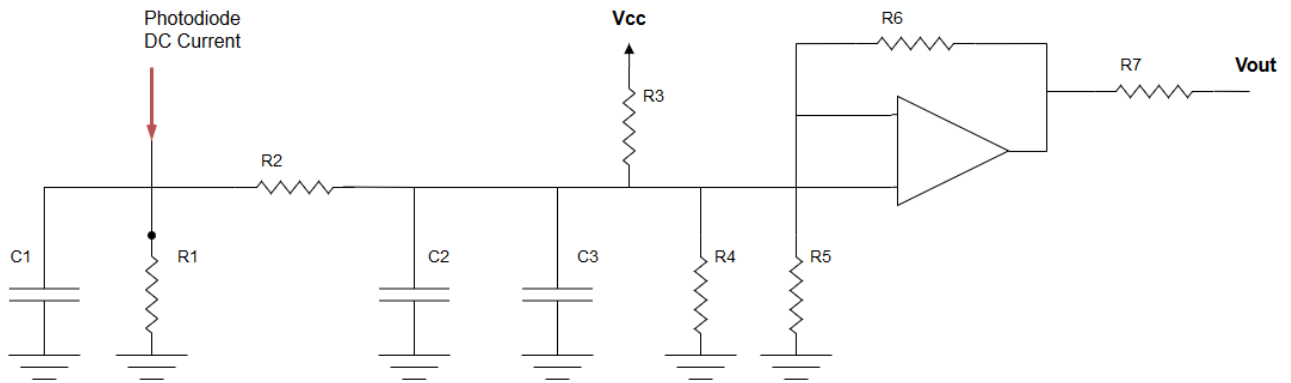This application performs an extreme value analysis of the following circuit (the principles, however, can be extended to any circuit). Light hits a photodiode and generates a current. A non-inverting op-amp then produces a linearly-proportional voltage from the photodiode current. Capacitors are ignored - hence this is a DC analysis.



| Component | Value                | Units    | Tolerance (%) |
|-----------|----------------------|----------|---------------|
| R1        | 900                  | $\Omega$ | 0.02          |
| R2        | 67500                | $\Omega$ | 0.02          |
| R3        | 2050000              | $\Omega$ | 0.01          |
| R4        | 89200                | $\Omega$ | 0.015         |
| R5        | 90000                | $\Omega$ | 0.015         |
| R6        | 87000                | $\Omega$ | 0.005         |
| R7        | 1.02                 | $\Omega$ | 0.07          |
| Vcc       | 3                    | V        | 0.01          |
| P         | $4.8 \times 10^{-4}$ | W        | 0.05          |

## ▼ Calculations

> restart:

Voltage generated by the op-amp

```

> Vout := proc(Rv)
  local R1, R2, R4, R3, R5, R6, R, Vcc, P:
  R1 := Rv[1]:
  R2 := Rv[2]:
  R3 := Rv[3]:
  R4 := Rv[4]:
  R5 := Rv[5]:
  R6 := Rv[6]:
  R := Rv[7]:
  Vcc := Rv[8]:
  P := Rv[9]:
  return (R * P * R1 * (1 / (1 / R4 + 1 / R3))) / ( R1 + R2 + 1
/ (1 / R4 + 1 / R3)) + Vcc / R3 * 1 / (1 / R4 + 1 / R3 + 1 / (R2
+ R1))) * (R5 + R6) / R5;

```

```
end proc:
```

Parameter values and percentage tolerances in the order R1, R2, R3, R4, R5, R6, R, Vcc, P

```
> Rv := [9000, 67500, 2050000, 89200, 90000, 87000, 1.02, 3,
0.00048]:
Delta := [0.02, 0.02, 0.01, 0.015, 0.015, 0.005, 0.07, 0.01,
0.05]:
```

v is a vector that contains the calculated voltages for every permutation of extreme tolerance values (there are  $2^9 = 512$  combinations of the two extreme parameter values for each of the nine components in the circuit).

```
> zeta := Vector(512, i -> 1 +~ subs(0 = -1, Bits:-Split(i, bits =
9)) *~ Delta):
```

```
v := Vector(512, i -> Vout(Rv *~ zeta[i]))
```

$$v := \begin{bmatrix} 4.257792241 \\ 4.039654773 \\ 4.190990302 \\ 4.103357215 \\ 4.257166458 \\ 4.038932838 \\ 4.190326462 \\ 4.159538866 \\ 4.315517230 \\ 4.095319584 \\ \vdots \end{bmatrix} \quad (2.1)$$

512 element Vector[column]

Hence the worst case minimum and maximum voltages are

```
> min(v);
max(v)
```

$$\begin{matrix} 3.979954450 \\ 5.485606376 \end{matrix} \quad (2.2)$$