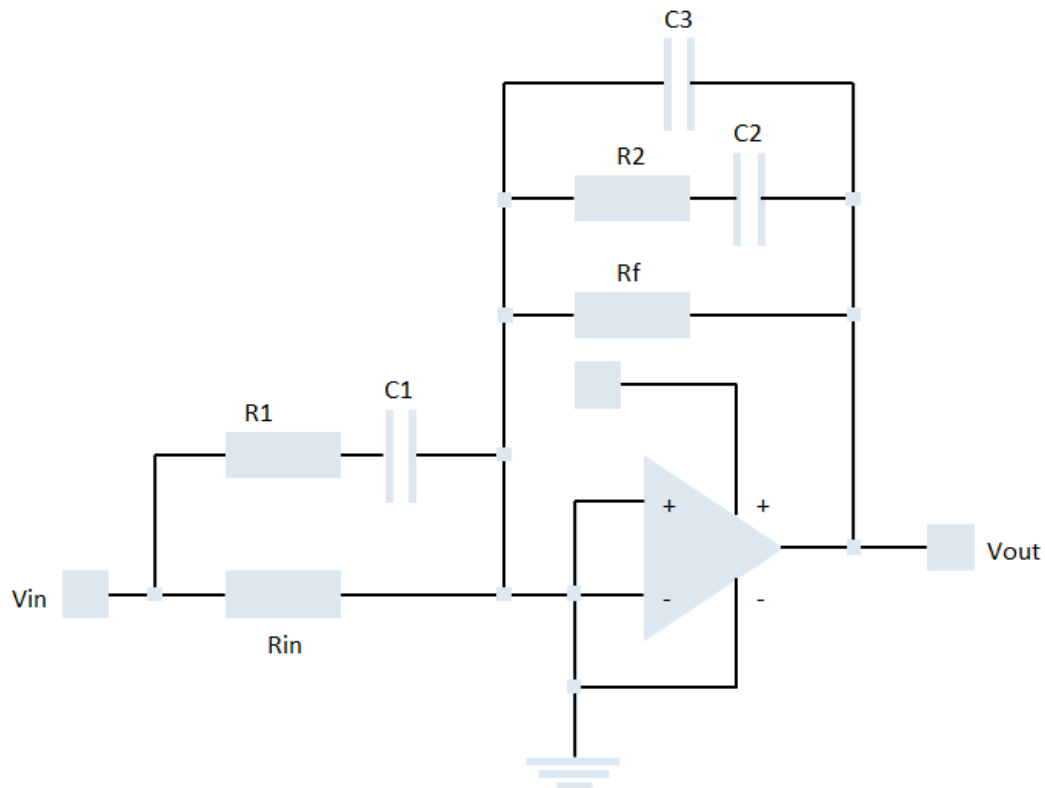


Amplifier Gain

▼ Introduction

In this application, we will plot the gain of the following amplifier circuit, for both the ideal and non-ideal response.



```
> restart :
  with( DynamicSystems ) :
  with( plots ) :
```

▼ Parameters

```
>  $R_1 := 1000 :$ 
>  $C_1 := 10^{-7} :$ 
```

$$> R_{In} := 1000 :$$

$$> C_3 := 4.7 \cdot 10^{-8} :$$

$$> R_2 := 1000 :$$

$$> C_2 := 4.70 \cdot 10^{-7} :$$

$$> R_f := 10^{102} :$$

Amplifier bandwidth factors:

$$> GBP := 10^6 :$$

$$> LPF := 300 :$$

▼ Support Function

$$> ll := (Z1, Z2) \rightarrow \frac{Z1 \cdot Z2}{Z1 + Z2} :$$

▼ Transfer functions

$$> Z_1 := R_1 + \frac{1}{s \cdot C_1} :$$

$$> Z_2 := R_2 + \frac{1}{s \cdot C_2} :$$

$$> Z_{In} := ll(R_{In}, Z_1) :$$

$$> \text{factor}(Z_{In})$$

$$\frac{500 (s + 10000)}{s + 5000}$$

(4.1)

$$> Z_{fb} := ll\left(R_f, ll\left(Z_2, \frac{1}{s \cdot C_3}\right)\right) :$$

Ideal amplifier gain:

$$> G_{EAideal} := \text{factor}\left(\frac{Z_{fb}}{Z_{In}}\right)$$

$$G_{EAideal} := \frac{42553.19148 (s + 2127.659574) (s + 5000.)}{(s + 1.934235977 \cdot 10^{-96}) (s + 23404.25531) (s + 10000.)}$$

(4.2)

Non-ideal op-amp effects: Finite open loop gain

$$> \beta := \frac{1}{1 + G_{EAideal}} :$$

Finite open loop gain

$$\begin{aligned}
 &> A_{vo} := \frac{GBP}{LPF} \cdot \frac{1}{\left(1 + \frac{s}{2 \cdot \pi \cdot LPF}\right) \cdot \left(1 + \frac{s}{2 \cdot \pi \cdot GBP}\right)} \\
 &A_{vo} := \frac{10000}{3 \left(1 + \frac{s}{600 \pi}\right) \left(1 + \frac{s}{2000000 \pi}\right)} \quad (4.3)
 \end{aligned}$$

> simplify((4.3), 'size')


$$\frac{4000000000000 \pi^2}{(600 \pi + s) (2000000 \pi + s)} \quad (4.4)$$

Non-ideal error amplifier gain:

$$\begin{aligned}
 &> G_{EA} := \text{simplify} \left(G_{EAideal} \cdot \frac{1}{1 + \frac{1}{A_{vo} \cdot \beta}} \right) \\
 &G_{EA} := \left(1.787162409 10^{25} + 1.679932664 10^{18} s^2 + 1.197398814 10^{22} s \right) / \\
 &\quad \left(5.36148722210544 10^{21} + s^5 + 6.36102770911571 10^6 s^4 + 3.99681963841567 10^{13} s^3 \right. \\
 &\quad \left. + 1.32302446297123 10^{18} s^2 + 9.24883894862041 10^{21} s \right) \quad (4.5)
 \end{aligned}$$

▼ Analysis

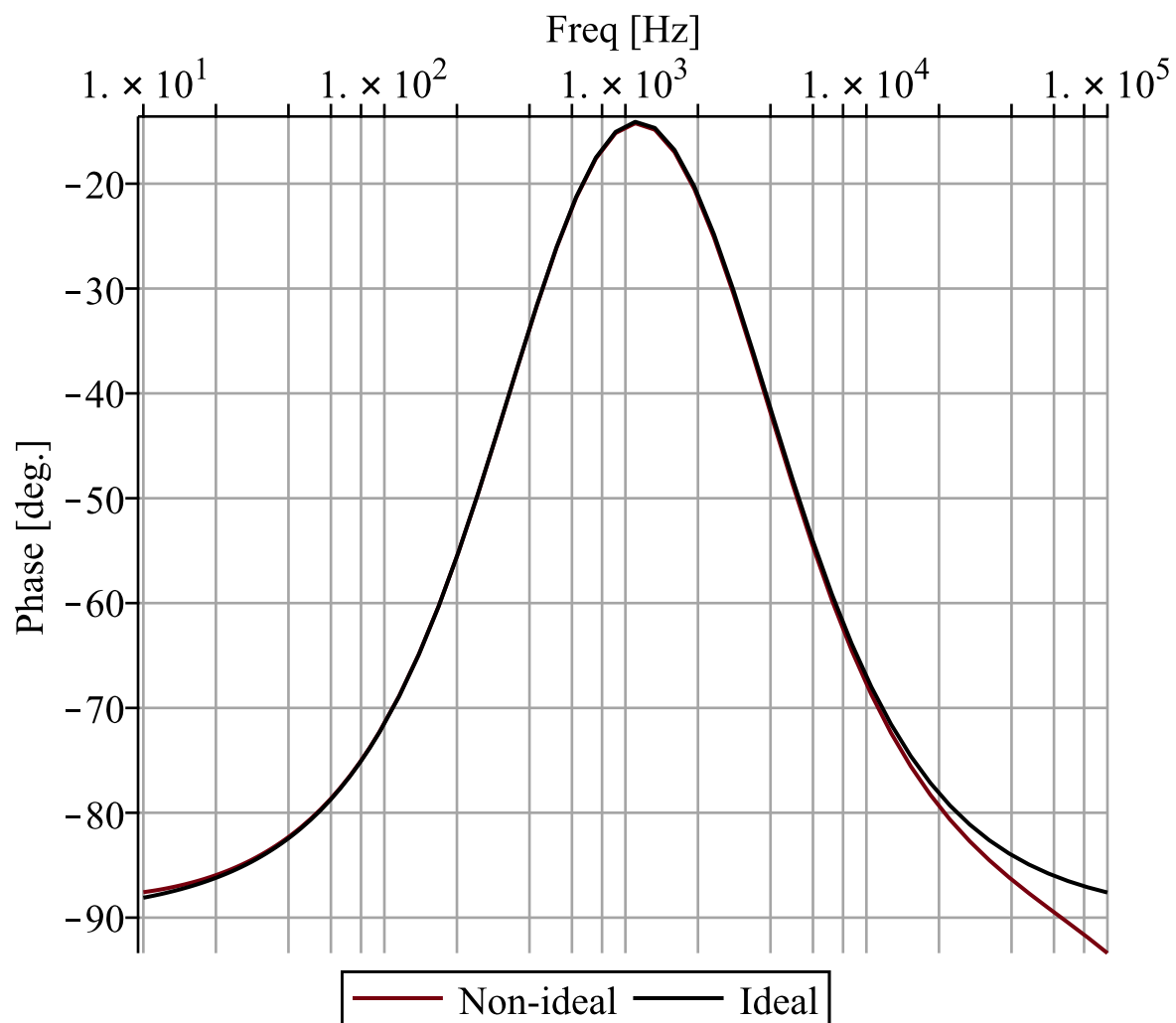- > sys1 := TransferFunction(G_{EA}) :
- > sys2 := TransferFunction($G_{EAideal}$) :
- > p1 := PhasePlot(sys1, range = 10 .. 100000, hertz = true, legend = "Non-ideal") :
- > p2 := PhasePlot(sys2, range = 10 .. 100000, hertz = true, legend = "Ideal", color = black) :
- > display(p1, p2)



>