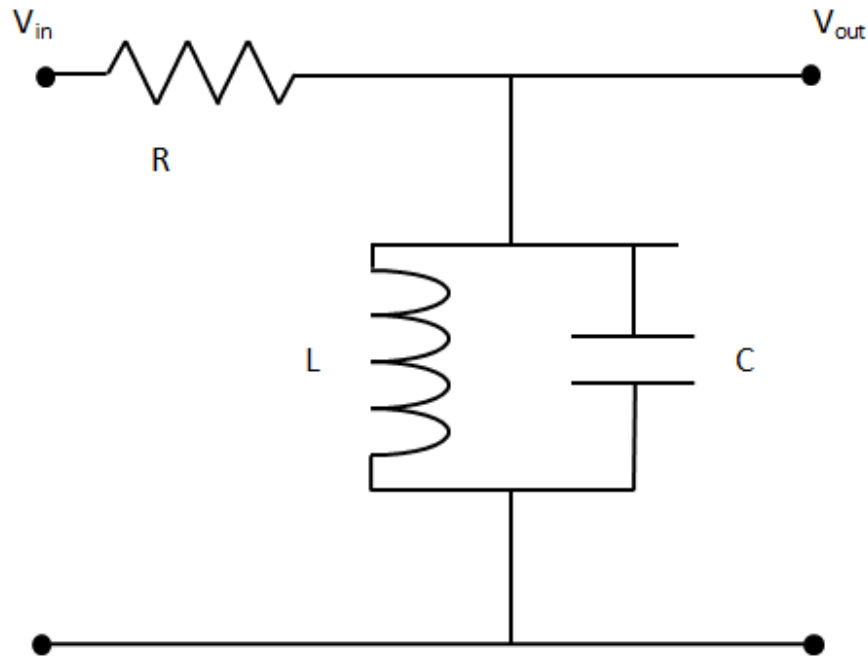


# Bandpass Filter Design



> *restart* :

This transfer function defines the response of a Bandpass filter.

$$> G := \frac{\frac{s}{RC}}{s^2 + \frac{s}{RC} + \frac{1}{LC}} :$$

The product  $L C$  controls the bandpass frequency while  $R C$  controls how narrow the passing band is. To build a bandpass filter tuned to the frequency 1 rad/s, set  $L=C=1$  and use  $R$  to tune the filter band.

First define a transfer function object.

> *with*(*DynamicSystems*) :

> *sysTF* := *TransferFunction*(*G*)


$sysTF :=$ 

Transfer Function
continuous
1 output(s); 1 input(s)
inputvariable = $[u1(s)]$
outputvariable = $[y1(s)]$

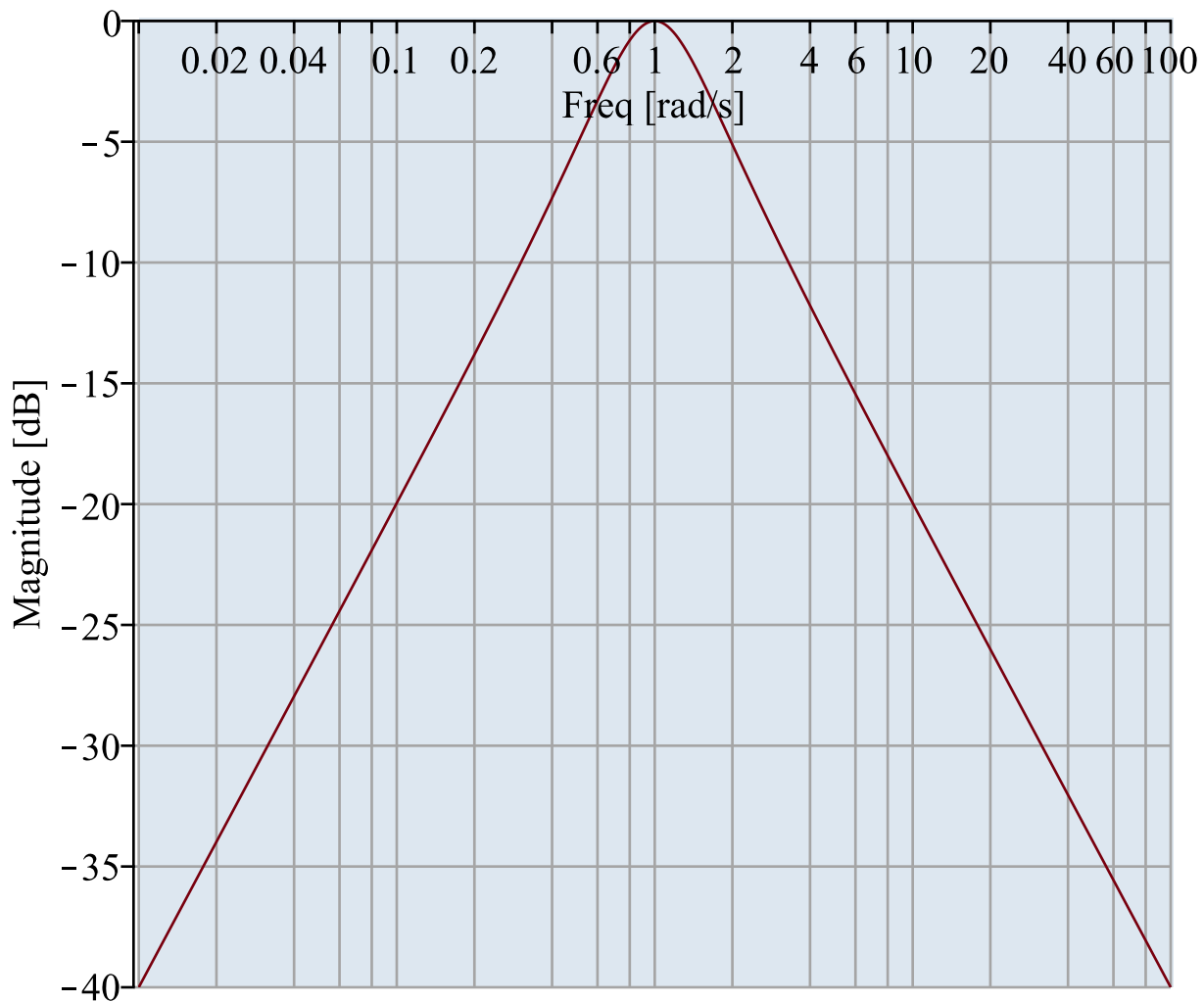(1)

Now generate a Magnitude plot


> `MagnitudePlot(sysTF, size = [800, 400], parameters = [R = 1, L = 1, C = 1], background = ColorTools:-Color("RGB", [221/255, 231/255, 240/255]), thickness = 0)`



As expected, the RLC filter has maximum gain at the frequency 1 rad/s. However, the attenuation is only -10dB half a decade away from this frequency.

To get a narrower passing band, try increasing values of R.
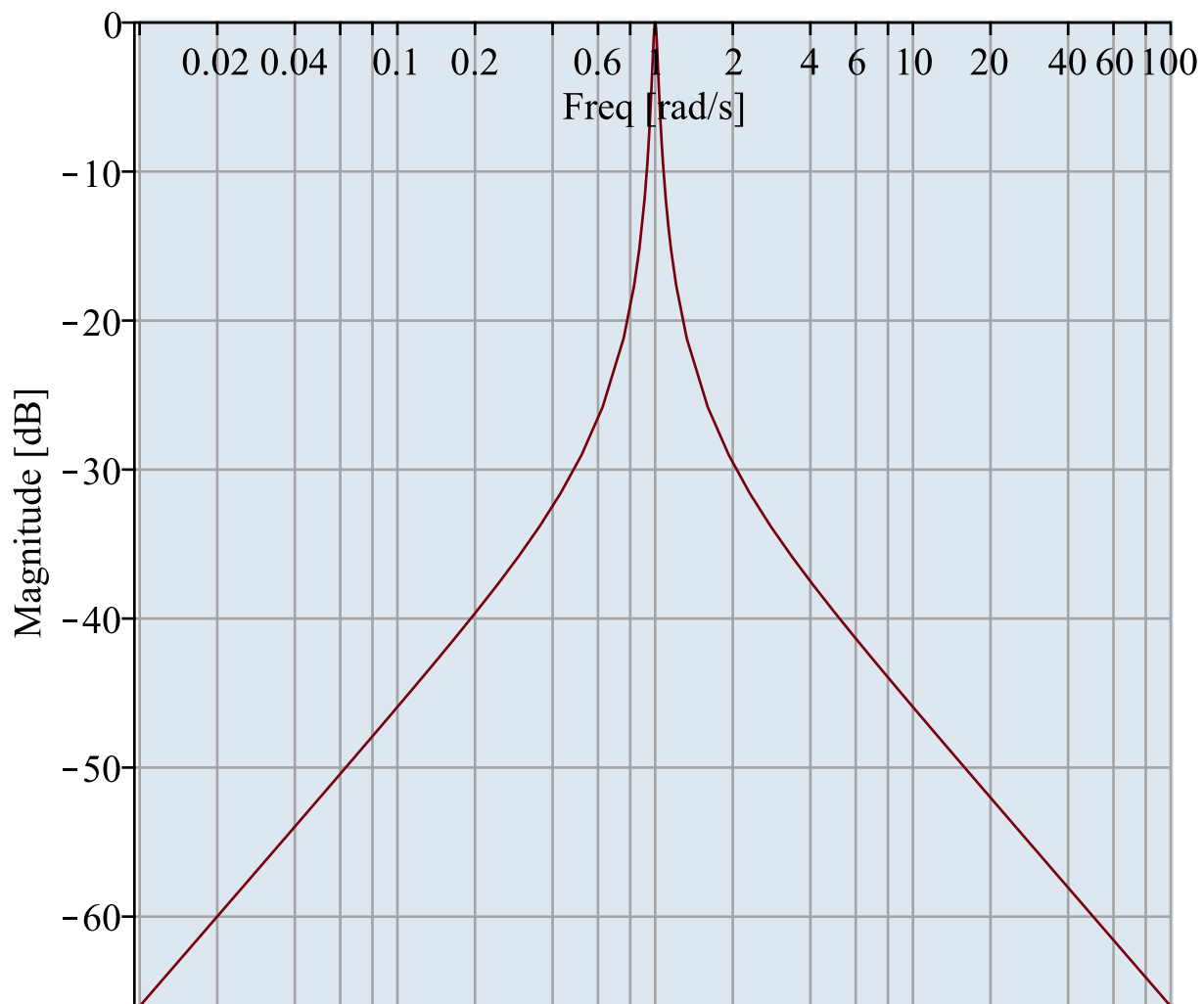
> `MagnitudePlot(sysTF, size = [800, 400], parameters = [R = 20, L = 1, C = 1], background = ColorTools:-Color("RGB", [221/255, 231/255, 240/255]), thickness = 0)`




The resistor value  $R=20$  gives a filter narrowly tuned around the target frequency of 1 rad/s.

We can confirm the attenuation properties of the circuit ( $R=20$ ) by simulating how this filter transforms sine waves with frequency 0.9, 1, and 1.1 rad/s.

Create two response plots for the filter at  $R=20$  with two inputs:  $\sin(0.9 t)$  and  $\sin(t)$ .

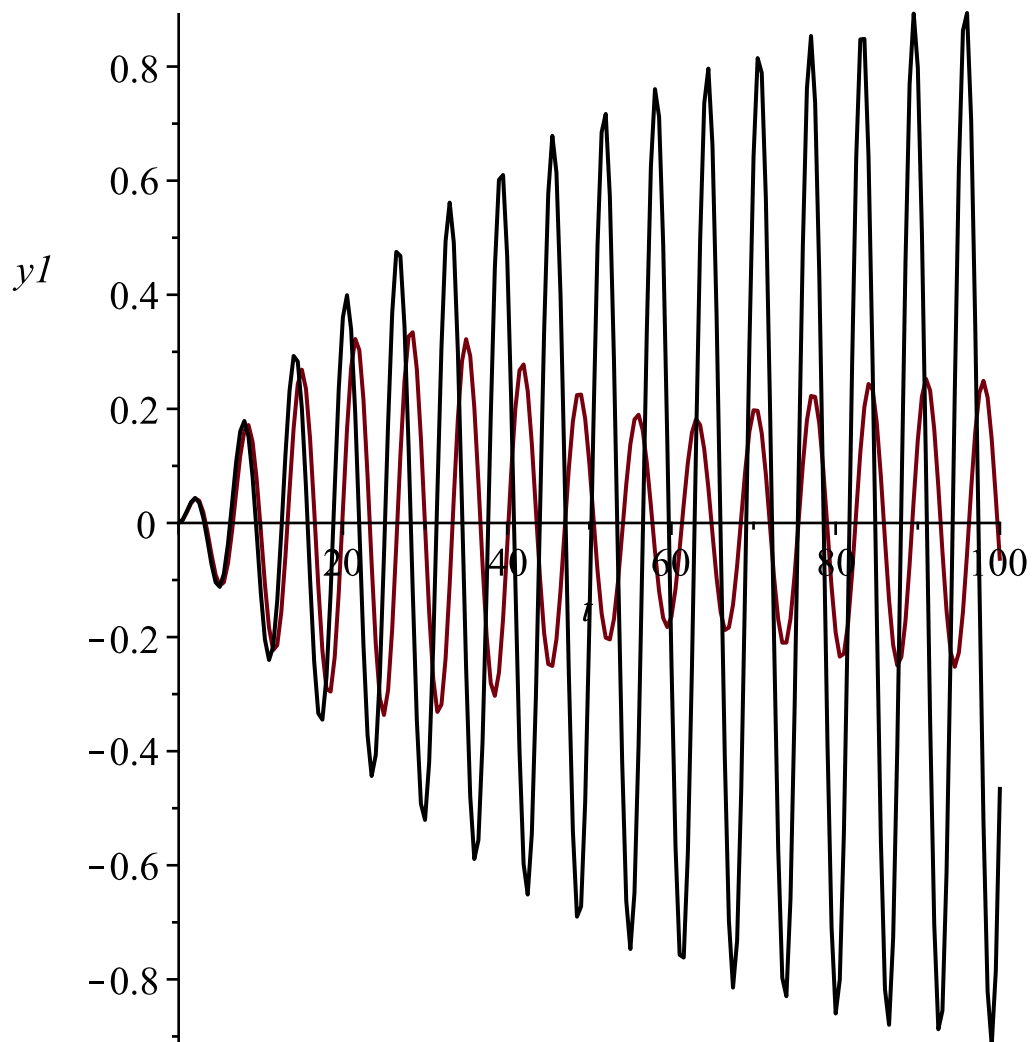- >  $p1 := \text{ResponsePlot}(\text{sysTF}, \sin(0.9 \cdot t), \text{duration} = 100, \text{parameters} = [R = 20, L = 1, C = 1]) :$
- >  $p2 := \text{ResponsePlot}(\text{sysTF}, \sin(t), \text{duration} = 100, \text{parameters} = [R = 20, L = 1, C = 1], \text{color} = \text{black}) :$
- >  $\text{plots:display}(p1, p2)$



>